

San Jose State University
Department of Computer Engineering

CMPE 200 Report

Assignment 1 Report

Title System-Level Design Review

Semester: Fall 2023

Date: 09/16/2023

by

Name: Sai Kashyap Kurella

SID: 016018925

FACTORIAL SYSTEM TOP LEVEL

 


Fig.1 Top level view of Factorial System

SYSTEM DATA PATH

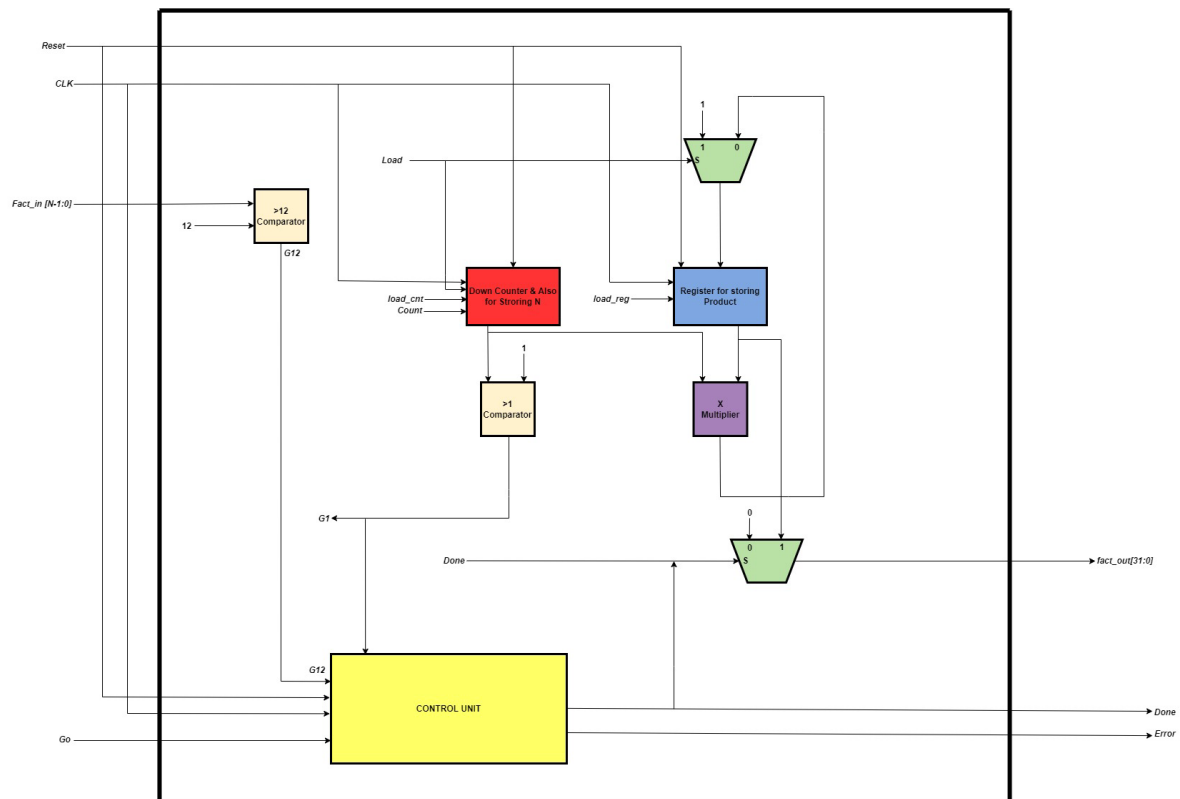


Fig.2 System Data Path with Control unit

Finite State Machine for Control Unit

 


Fig.3 State Transitions of Control unit

ASM chart for Control Unit

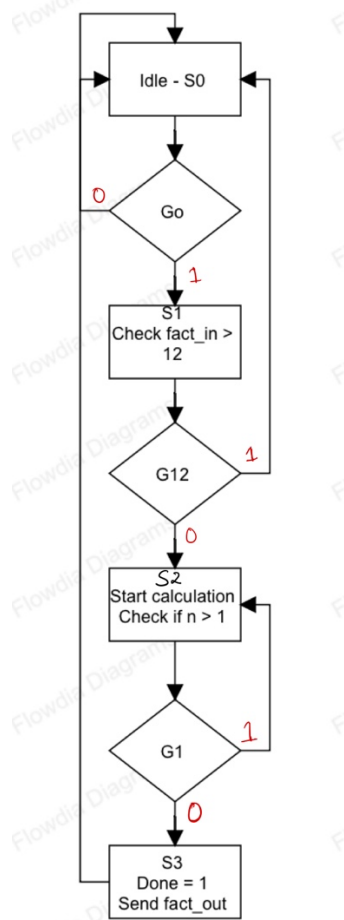


Fig.4 State transitions in ASM chart

Verilog Codes of Individual Modules

Counter

```
module CNT # (parameter N=4)
(
input clk,
input reset,
input en,
input load_cnt,
input [N-1:0] load_value,
output[N-1:0] count_q
);
reg[N-1:0] load_ff;
```

```

//Store the load Value whenever load_cnt is seen
always@(posedge clk or posedge reset)
    begin
        if(reset)
            begin
                load_ff <= 4'h0;
            end
        else if(load_cnt)
            begin
                load_ff <= load_value;
            end
        else
            begin
                load_ff <= load_ff;
            end
        end
    reg[3:0] count_ff;
    reg[3:0] nxt_count;

always@(posedge clk or posedge reset)
    begin
        if(reset)
            begin
                count_ff <= 4'hF;
            end
        else
            begin
                if(en)
                    begin
                        count_ff <= nxt_count;
                    end
                else
                    begin
                        count_ff <= count_ff;
                    end
            end
        end
    end

assign nxt_count = load_cnt ? load_value : (count_ff == 4'h0) ? load_ff : count_ff - 4'h1;

//assign nxt_count = (count_ff == 4'h0) ? load_ff : count_ff - 1'h1;

assign count_q = count_ff;

endmodule

```

Comparator

```
module CMP #(parameter N = 4)
(
input [N-1:0] A,
input [N-1:0] B,
output G
);

assign G = (A>B) ? 1'b1: 1'b0;

endmodule
```

Multiplier

```
module MUL(input[3:0] A, input[31:0] B, output[31:0] O);

assign O = A*B;

endmodule
```

Multiplexer

```
module MUX #(parameter N =1 )
(
input [31:0] A,
input [31:0] B,
input S,
output [31:0] Y
);
assign Y = (S) ? B : A ;
endmodule
```

Data register with a load control signal

```
module REG #(parameter N = 4)
(
input clk,
input reset,
input load_reg,
input [31:0] reg_d,
output [31:0] reg_q
);
```

```

reg[31:0] store_reg;

//Sequential Block
always@(posedge clk or posedge reset)
    begin
        if(reset)
            begin
                store_reg <= 32'h1;
            end

        else
            begin
                if(load_reg)
                    begin
                        store_reg <= reg_d;
                    end

                else
                    begin
                        store_reg <= 32'h1;
                    end
            end
        end

    end

//Combinational Block
assign reg_q = store_reg;

endmodule

```

Control Unit

```

module Control
(
    input clk,
    input reset,
    input Go,
    input G1,
    input G12,

```

```
output reg Error,

output reg load_cnt,

output reg Done_cntrl,

output reg load_reg,

output reg count

);

parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

reg[1:0] present_state;

reg[1:0] next_state;

//Sequential Part

always@(posedge clk or posedge reset)

begin

    if(reset)

        begin

            present_state <= S0;

        end

    else

        begin

            present_state <= next_state;

        end

end

//Combinational Part

always@(*)
```



```

begin
case(present_state)
    S0 :    begin                                // Initial Stage

        Error = 1'b0;

        load_cnt = 1'b0;

        Done_cntrl = 1'b0;

        count = 1'b0;

        load_reg = 1'b0;

        if(Go)
            begin
                next_state = S1;
            end
        else
            begin
                next_state = S0;
            end
        end

    S1 :    begin                                // Check if input is > 12

        if(G12)
            begin
                next_state = S0;

                Error = 1'b1;
            end
        end
    end
end

```

```
        end  
  
    else  
  
        begin  
  
            next_state = S2;  
  
            load_cnt = 1'b1;  
  
            count = 1'b1;  
  
        end  
  
    end  
  
S2 :   begin                                     //Calculation Stage  
  
        load_cnt = 1'b0;  
  
        if(G1)  
  
            begin  
  
                next_state = S2;  
  
                load_reg = 1'b1;  
  
            end  
  
        else  
  
            begin  
  
                next_state = S3;  
  
                count = 1'b0;  
  
            end  
  
        end  
  
end  
  
S3 :   begin                                     //Done  
  
        next_state = S0;
```

```
        Done_cntrl = 1'b1;
```

```
    end
```

```
endcase
```

```
end
```

```
endmodule
```

Top Level module

```
`include "CMP.v"
```

```
`include "CNT.v"
```

```
`include "MUL.v"
```

```
`include "REG.v"
```

```
`include "MUX.v"
```

```
`include "Control.v"
```

```
module Top #(parameter N = 4) (
```

```
    input clk,
```

```
    input reset,
```

```
    input Go,
```

```
    input [N-1:0] fact_in,
```

```
    output [31:0] fact_out,
```

```
    output Done,
```

```
    output Error
```

```
);
```

```
    wire load_cnt; //Control
```

```

wire load_reg; //Control

wire count; //Control

wire[N-1:0] count_q;

wire G1; //Control

wire[31:0] reg_d;

wire[31:0] reg_q;

wire[31:0] O;

wire G12; //Control

wire done; //Control

//Comparator-1 (for checking >1)

CMP c1(.A(count_q),.B(4'h1),.G(G1));


//Counter

CNT
cnt1(.clk(clk),.reset(reset),.en(count),.load_cnt(load_cnt),.load_value(fact_in),.count_q(count_q)
);

//Multiplier

MUL mul1(.A(count_q),.B(reg_q),.O(O));

//Data register with a load control signal

REG reg1(.clk(clk),.reset(reset),.load_reg(load_reg),.reg_d(reg_d),.reg_q(reg_q));

//Multiplexer-1

MUX mux1(.A(O),.B(32'h1),.S(load_cnt),.Y(reg_d));

//Multiplexer-2 (Buffer)

```

```

MUX mux2(.A(32'h0),.B(reg_q),.S(done),.Y(fact_out));

//Comparator-2 (for checking >12)

CMP c2(.A(fact_in),.B(4'hC),.G(G12));

//Controller

Control
ctrl(.clk(clk),.reset(reset),.Go(Go),.G1(G1),.G12(G12),.Error(Error),.load_cnt(load_cnt),.load_reg(load_reg),.Done_cntrl(done),.count(count));

assign Done = done;

endmodule

```

Top Level Test Bench

```

module Top_tb#(parameter N = 4)();

reg clk;

reg reset;

reg Go;

reg [N-1:0] fact_in;

wire[31:0] fact_out;

wire Done;

wire Error;

```

```
Top
t1(.clk(clk),.reset(reset),.Go(Go),.fact_in(fact_in),.fact_out(fact_out),.Done(Done),.Error(Error)
);

// Clock Generation

always

begin

    clk = 1'b1;

    #2;

    clk = 1'b0;

    #2;

end

// Stimulus

initial

begin

    reset = 1'b1;

    fact_in = 4'hC;

    Go = 1'b0;

    @(posedge clk);

    reset = 1'b0;

    Go = 1'b1;

    @(posedge clk);

    Go = 1'b0;

    #100;

    fact_in = 4'h8;
```

```

        @(posedge clk);

        Go = 1'b1;

        @(posedge clk);

        Go = 1'b0;

        #100;

        fact_in = 4'hF;

        @(posedge clk);

        Go = 1'b1;

        @(posedge clk);

        Go = 1'b0;

        #100;

        $finish;

end

initial
begin

    $monitor ("Result = %b", fact_out);

    $dumpfile ("factorial_waves.vcd");

    $dumpvars();


end

endmodule


```

Simulations:


I. For fact_in = 12

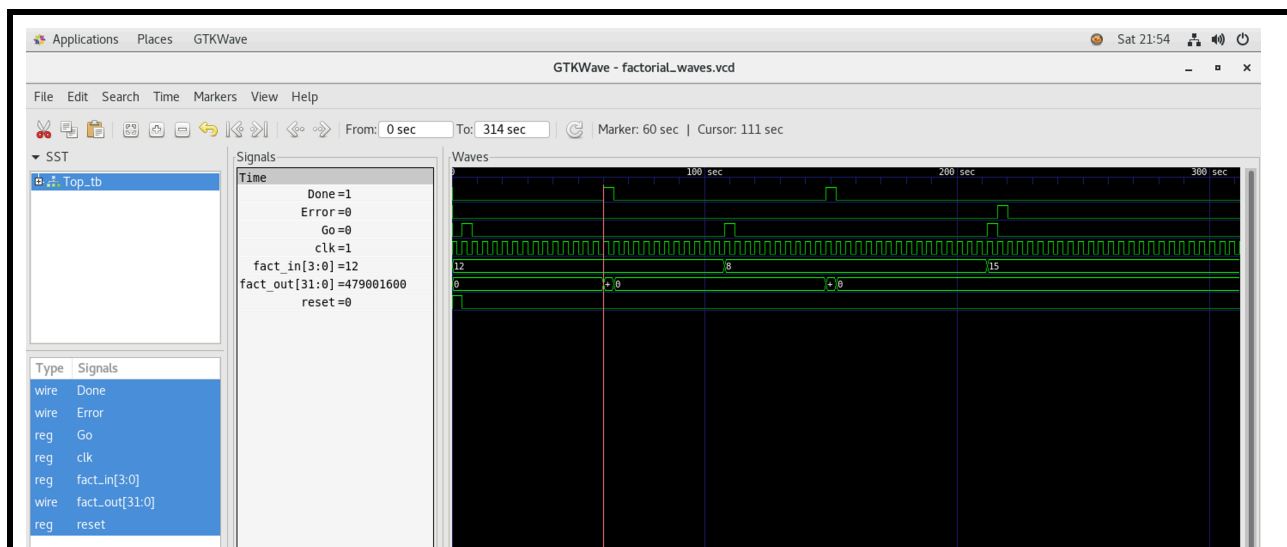

II. For fact_in = 8

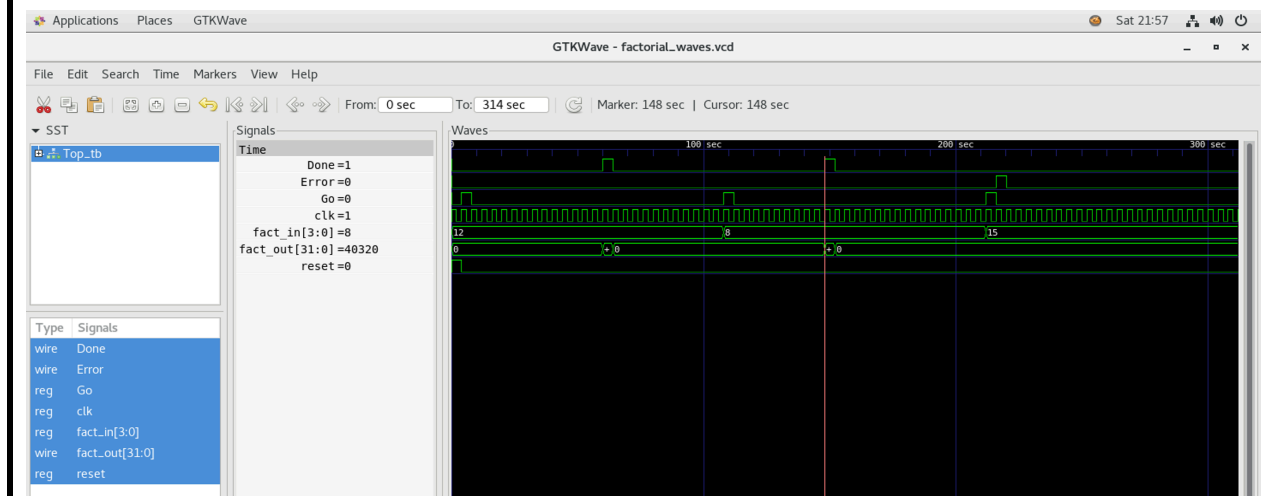

III. For fact_in = 16

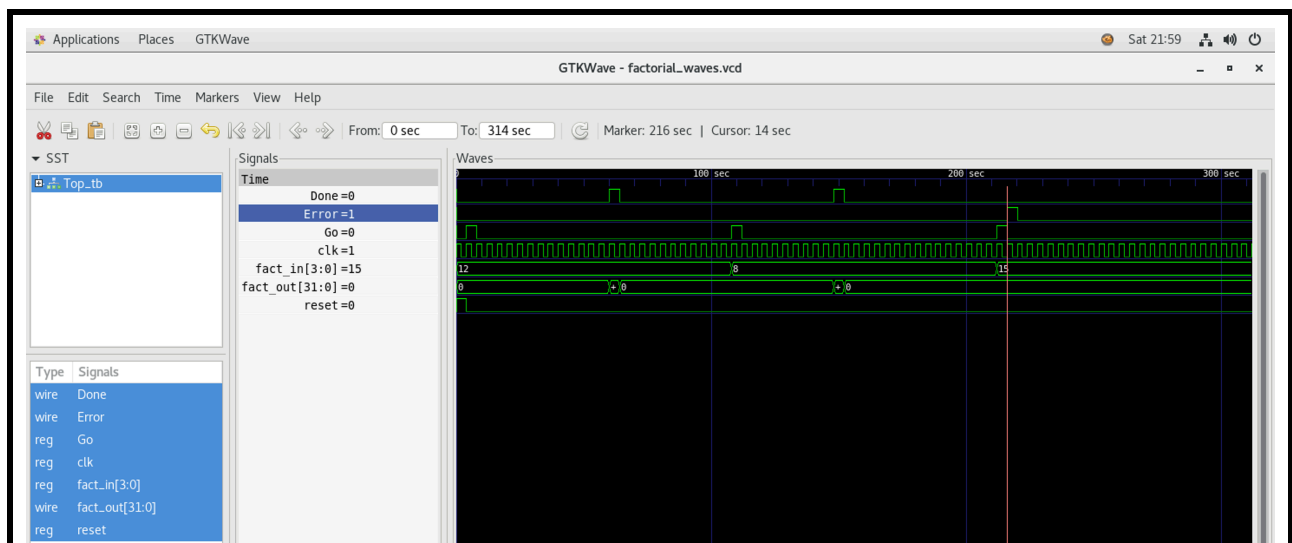

Conclusion

The data-path and the control unit for the factorial system has been designed and verified for all the cases as shown above. All the verilog design files have been submitted along with the report.